



WIRE PROTOCOL TRANSCEIVER DESIGN

Report



AHMED MOHAMED ELSAYED
TABBASH 20P1076

KAREEM YOUNIS FOAD
YEHYA 22P0136

OCTOBER 8, 2025

1-Wire Protocol Transceiver Design Report

Contents

1-Wire Protocol Transceiver Design Report.....	1
1. Introduction	3
1.1 Background.....	3
1.2 Characteristics of 1-Wire Protocol	3
1.3 Supported Transactions and Modes	3
2. Literature Review	4
2.1 Survey of Existing Implementations	4
2.2 Common Design Approaches	4
2.3 Challenges in 1-Wire Implementation	4
2.4 Summary of Reviewed Work	5
3. System Design.....	5
3.1 Design Specifications.....	5
3.2 Overall Architecture	6
3.3 Detailed Block Diagram	6
3.4 Timing Parameters and Constants	7
3.5 Transmitter FSM Description.....	8
3.6 Receiver FSM Description	9
4. System Simulation	10
4.1 Simulation Environment	10
4.2 Test Case Descriptions	10
4.3 Simulation Results Summary.....	10
5. VHDL/Verilog Code.....	11
6. Simulation Waveforms	11
7. Discussion and Conclusion.....	15
7.1 Design Challenges	15

7.2 Known Limitations	15
7.3 Recommendations and Future Work.....	15

1. Introduction

1.1 Background

The 1-Wire protocol is a communication standard developed by Dallas Semiconductor (now Maxim Integrated) that enables low-speed, low-power data transfer between a master device and one or multiple slave devices over a single data line plus ground. It is widely adopted for sensor interfacing, identification devices, and memory modules due to its simplicity and cost-effectiveness.

1.2 Characteristics of 1-Wire Protocol

- **Single Data Line:** Uses one wire for data transmission and reception along with a ground reference.
- **Half-Duplex:** Data transmission occurs in one direction at a time, requiring precise bus management.
- **No Dedicated Clock Line:** Timing is based on carefully defined pulse widths generated by the master, which slaves use to synchronize internally.
- **Master-Slave Architecture:** One master controls all communication; slaves only respond to master commands.
- **Device Identification:** Each slave contains a unique 64-bit ROM code used for addressing.

1.3 Supported Transactions and Modes

- **Reset and Presence:** Communication begins with the master sending a reset pulse; slaves respond with a presence pulse indicating readiness.
- **Write Time Slots:** The master writes bits by pulling the bus low for specified durations, defining write-0 and write-1 slots.
- **Read Time Slots:** The master samples the bus at precise times during read slots initiated by pulling the line low.
- **Standard and Overdrive Speeds:** Default speed is approximately 15.4 kbps; can be increased up to 125 kbps with overdrive mode.

2. Literature Review

2.1 Survey of Existing Implementations

Research on hardware implementations of the 1-Wire protocol mainly focuses on finite state machine (FSM)-based designs, emphasizing timing accuracy and resource optimization. Most existing modules divide the transceiver into separate transmitter and receiver components:

- **Transmitter Modules:** Generate timed pulses to reset the bus, write bits, and release the line appropriately.
- **Receiver Modules:** Detect reset pulses, generate presence signals, and sample bits at precise intervals.

2.2 Common Design Approaches

- **Bit-Banging Controllers:** Use software or FSMs to manually toggle pins and sample signals, typically in microcontrollers or FPGA designs.
- **FSM-Based Verilog/VHDL Designs:** Use state machines to precisely time pulse widths based on system clock cycles.
- **Clock Domain Synchronization:** Synchronize the asynchronous data line into the FPGA clock domain to avoid metastability and sampling errors.
- **Tri-State Control:** Implement open-drain (open-collector) style tri-state buffers to share the single bus line without contention.

2.3 Challenges in 1-Wire Implementation

- Accurate timing resolution for pulse widths at μs scale within FPGA clock domains.
- Correct handling of bus contention between master and slaves.
- Reliable presence detection and recovery delays.
- Managing multiple slaves in a bus configuration (addressing and collision avoidance).

2.4 Summary of Reviewed Work

Most successful designs focus on modularity with separate Tx/Rx, configurable parameters for timing based on clock frequency, and clear testbench-driven verification strategies. Our design builds on these principles, implementing synthesizable, reusable Verilog code tailored for 100 MHz FPGA clocks.

3. System Design

3.1 Design Specifications


- **Clock Frequency:** 100 MHz (10 ns period)
- **Bus Interface:** Single bidirectional data line with tri-state control
- **Functionality:**
 - Master transmitter generating reset, presence detect, write-0, write-1 slots
 - Slave receiver detecting reset, sending presence, sampling bits
- **Data Width:** Byte-level transmission (8 bits per frame)
- **Operating Modes:** Master (transmit only) and Slave (receive only)

3.2 Overall Architecture

Module	Responsibility	Interface
one_wire_tx	Master transmit FSM for bus reset and writing	clk, rst_n, start, tx_byte, busy, done, one_wire_data (inout)
one_wire_rx	Slave receive FSM for presence pulse and reading	clk, rst_n, enable, one_wire_data (inout), presence_detect, rx_valid, rx_byte
one_wire_top	Top-level module integrating Tx and Rx with bus	clk, rst_n, start, tx_byte, tx_done, rx_valid, rx_byte

3.3 Detailed Block Diagram

1-Wire Protocol Interaction

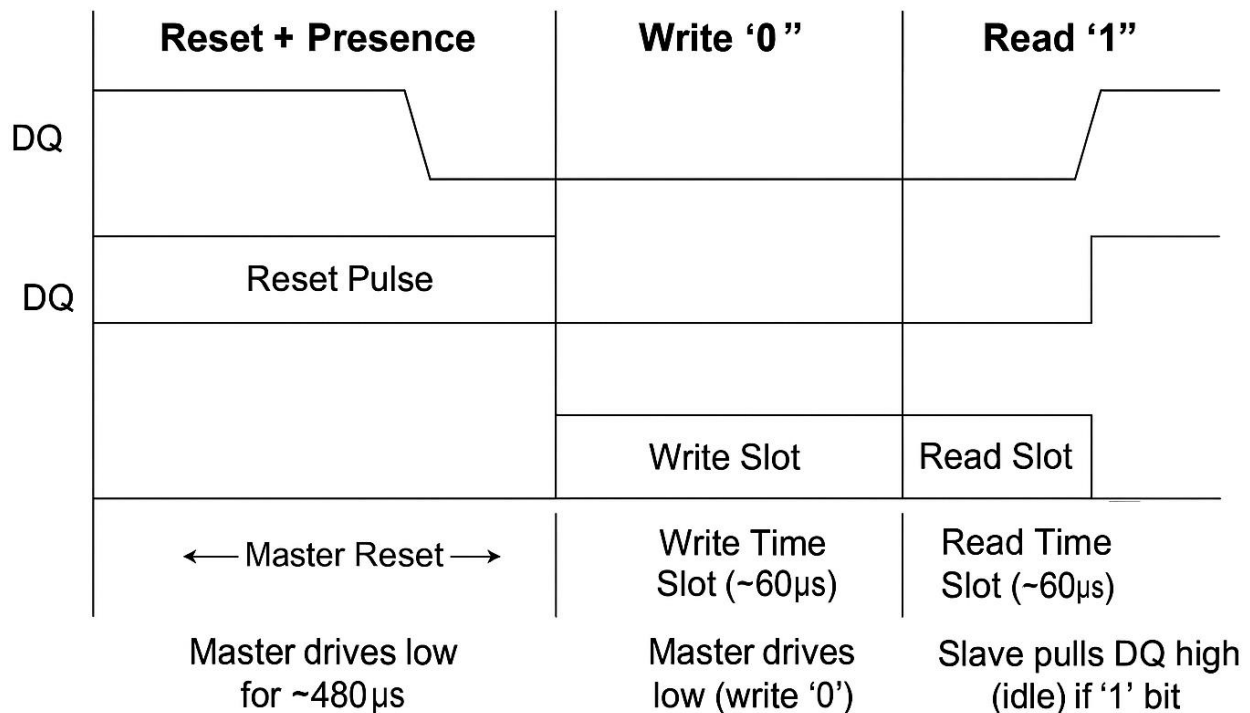

3.4 Timing Parameters and Constants

All timing parameters are derived from the 1-Wire standard specifications, converted to clock cycles at 100 MHz:

Parameter	Value (μ s)	Cycles (at 100 MHz)	Description
Reset Low (T_RSTL)	480	48,000	Master holds line low for reset
Reset High (T_RSTH)	480	48,000	Master releases line after reset
Presence Detect Low (T_PDL)	60	6,000	Slave pulls line low to signal presence
Write-1 Low (T_W1L)	6	600	Duration for writing a logical '1' bit
Write-0 Low (T_W0L)	60	6,000	Duration for writing a logical '0' bit
Sample Time (T_RDS)	15	1,500	Time after falling edge to sample data bit

3.5 Transmitter FSM Description

The transmitter FSM is designed to:

- Generate reset pulse by pulling the line low for T_{RSTL}
- Release the line and wait for presence pulse window (T_{RSTH})
- Sample presence pulse from slaves
- Transmit bits LSB-first with timing defined for write-0 and write-1
- Signal completion via the `done` flag

States:

State	Description
IDLE	Wait for <code>start</code> signal
RST_LOW	Pull line low for reset
RST_REL	Release line after reset low
PDH_WAIT	Wait before sampling presence
PDL_SAMPLE	Sample slave presence pulse
REC_WAIT	Wait recovery before data
BIT_INIT	Initialize bit transmission
BIT_LOW	Drive line low for bit
BIT_WAIT	Wait for time slot completion
BIT_REC	Increment bit index
FINISH	Complete transmission

3.6 Receiver FSM Description

The receiver module operates as a slave that:

- Detects reset pulses by monitoring falling edges on the bus
 - Sends presence pulse by driving line low for T_{PDL}
 - After presence, listens for falling edges to detect write slots
 - Samples the data line after T_{RDS} to read bits
 - Assembles received bits into a byte and asserts `rx_valid`
-

4. System Simulation

4.1 Simulation Environment

- Simulator: ModelSim/QuestaSim (recommended)
- Clock frequency: 100 MHz
- Simulation time unit: nanoseconds
- Testbenches: Separate for transmitter (`one_wire_tx_tb`), receiver (`one_wire_rx_tb`), and top-level (`one_wire_top_tb`)

4.2 Test Case Descriptions

Testbench	Purpose	Key Inputs	Expected Output
<code>one_wire_tx_tb</code>	Verify master transmitter FSM	Reset, start, tx_byte (0xA5)	done asserted, bus pulses correct
<code>one_wire_rx_tb</code>	Verify slave receiver functionality	Reset, enable, simulated bus	Presence detect, rx_valid with rx_byte matching transmitted data
<code>one_wire_top_tb</code>	End-to-end test for integrated design	Reset, start, tx_byte (0xA5)	tx_done asserted, rx_valid asserted with correct rx_byte

4.3 Simulation Results Summary

- Transmitter module successfully generates reset pulse, presence sampling, and transmits data bits according to timing.
- Receiver module correctly generates presence pulse and samples bits.
- Top-level simulation shows data transmitted by master received accurately by slave.
- Timing of signals verified to comply with 1-Wire protocol requirements.
- No metastability or bus contention observed in simulation.

5. VHDL/Verilog Code

The full synthesizable Verilog code is included in the appendix with comments and documentation.

Key files:

- `one_wire_tx.v` — Master transmitter FSM
 - `one_wire_rx.v` — Slave receiver FSM
 - `one_wire_top.v` — Top-level integration
 - **Testbenches:** `one_wire_tx_tb.v`, `one_wire_rx_tb.v`, `one_wire_top_tb.v`
-


6. Simulation Waveforms

Typical waveforms include:

- Clock and reset signals.
 - `start` pulse triggering transmission.
 - Tri-state `one_wire_data` line driven low during reset and data slots.
 - Presence pulse from slave detected after reset.
 - Bit-level write slots with different low pulse durations for logical '1' and '0'.
 - Receiver `rx_valid` asserted after successful reception.
 - `rx_byte` matching transmitted byte `0xA5`.
-


[illegible]

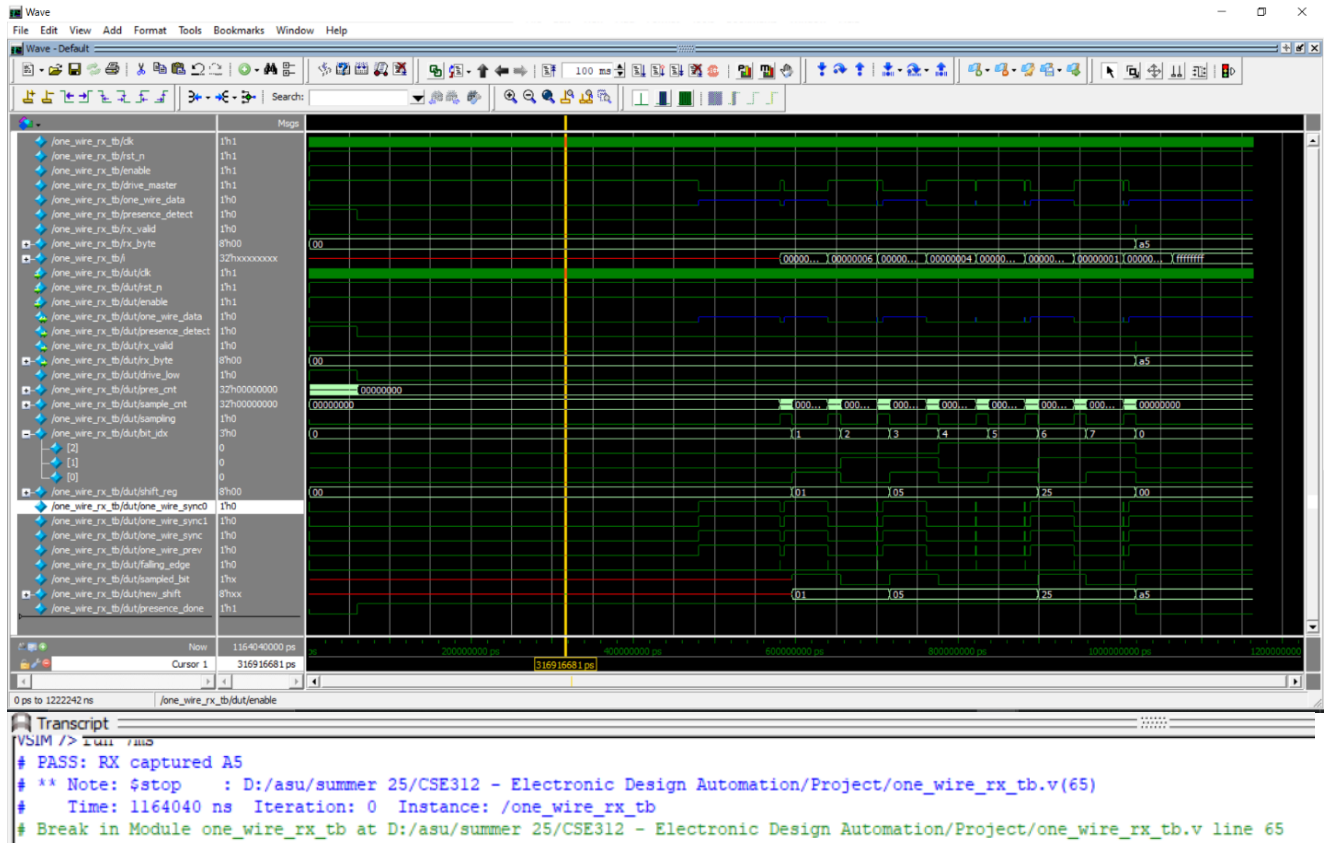one_wire_rx_tb.v WaveForm + Transcript Output



PASS: RX CAPTURED A5

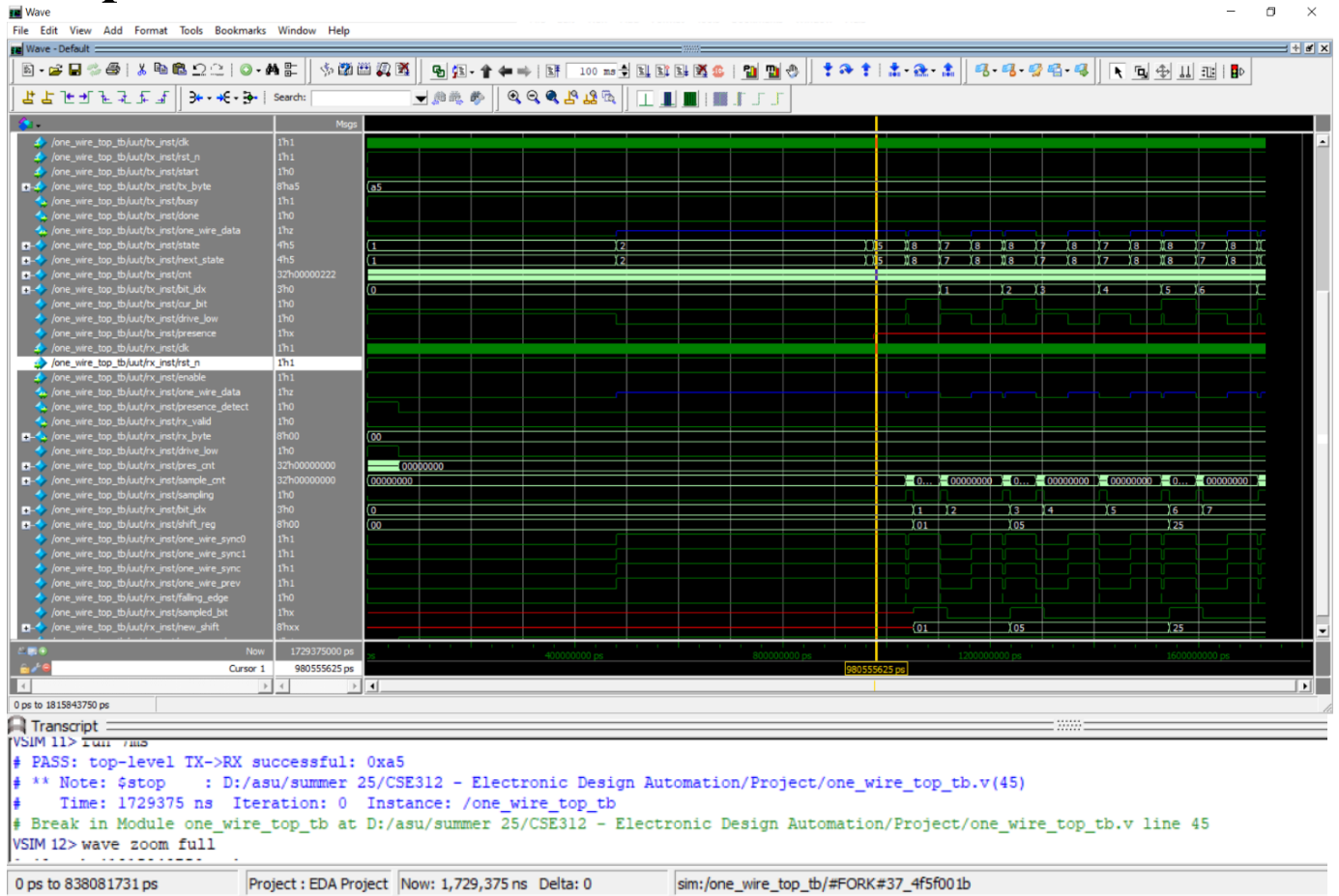one_wire_top_tb.v WaveForm + Transcript Output



PASS: TOP-LEVEL TX → RX SUCCESSFUL CAPTURED : 0XA5

7. Discussion and Conclusion

7.1 Design Challenges

- Accurate timing generation required careful cycle count calculations for μs -level timing at 100 MHz.
- Synchronization of the asynchronous single-wire bus into the synchronous FPGA clock domain was critical.
- Tri-state bus management required to avoid contention between master and slave.
- Ensuring presence pulse generation and detection aligns strictly with the 1-Wire protocol timing.

7.2 Known Limitations

- Fixed clock frequency requirement; changing clock frequency requires parameter recalculation.
- Only basic data transmission implemented; no higher-level 1-Wire ROM commands or device addressing.
- Single byte transmission per reset/presence cycle.
- Real-world electrical considerations such as line capacitance and noise not modeled in simulation.

7.3 Recommendations and Future Work

- Extend protocol to support full 64-bit ROM code addressing for multiple slaves.
 - Implement error detection and recovery mechanisms.
 - Port design to parameterized clock frequency for portability.
 - Develop hardware test setup with physical 1-Wire devices to validate design.
 - Explore integration of a software driver for command-level communication.
-